

# Solution of fundamental of electric circuits

Business, Industries



Chapter 1, Problem 1 How many coulombs are represented by these amounts of electrons: (a)  $6.482 \times 10^{17}$  (b)  $1.24 \times 10^{18}$  (c)  $2.46 \times 10^{19}$  (d)  $1.628 \times 10^{20}$  Chapter 1, Solution 1 (a)  $q = 6.482 \times 10^{17} \times [-1.602 \times 10^{-19} \text{ C}] = -0.10384 \text{ C}$  (b)  $q = 1.24 \times 10^{18} \times [-1.602 \times 10^{-19} \text{ C}] = -0.19865 \text{ C}$  (c)  $q = 2.46 \times 10^{19} \times [-1.602 \times 10^{-19} \text{ C}] = -3.941 \text{ C}$  (d)  $q = 1.628 \times 10^{20} \times [-1.602 \times 10^{-19} \text{ C}] = -26.08 \text{ C}$  Chapter 1, Problem 2. Determine the current flowing through an element if the charge flow is given by (a)  $q(t) = (3t + 8) \text{ mC}$  (b)  $q(t) = (8t^2 + 4t - 2) \text{ C}$  (c)  $q(t) = 3e^{-t} + 5e^{-2t} \text{ nC}$  (d)  $q(t) = 10 \sin 120t \text{ pC}$  (e)  $q(t) = 20e^{-4t} \cos 50t \text{ C}$  Chapter 1, Solution 2 (a) (b) (c) (d) (e)  $i = dq/dt = 3 \text{ mA}$   $i = dq/dt = (16t + 4) \text{ A}$   $i = dq/dt = (-3e^{-t} + 10e^{-2t}) \text{ nA}$   $i = dq/dt = 1200 \cos 120t \text{ pA}$   $i = dq/dt = -4e^{-4t} (80 \cos 50t + 1000 \sin 50t) \text{ A}$  A PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 1, Problem 3. Find the charge  $q(t)$  flowing through a device if the current is: (a)  $i(t) = 3 \text{ A}$ ,  $q(0) = 1 \text{ C}$  (b)  $i(t) = (2t + 5) \text{ mA}$ ,  $q(0) = 0$  (c)  $i(t) = 20 \cos(10t + \pi/6) \text{ A}$ ,  $q(0) = 2 \text{ C}$  (d)  $i(t) = 10e^{-30t} \sin 40t \text{ A}$ ,  $q(0) = 0$  Chapter 1, Solution 3 (a)  $q(t) = \int i(t) dt + q(0) = (3t + 1) \text{ C}$  (b)  $q(t) = \int (2t + 5) dt + q(0) = (t^2 + 5t) \text{ mC}$   $q(t) = \int 10e^{-30t} \sin 40t dt + q(0) = (c) q(t) = \int 20 \cos(10t + \pi/6) dt + q(0) = (2 \sin(10t + \pi/6) + 1) \text{ C}$  (d)  $10e^{-30t} (\int 0 \sin 40t dt - 40 \cos t) 900 + 1600 = -30t (0.16 \cos 40t + 0.12 \sin 40t) \text{ C}$  Chapter

1, Problem 4. A current of 3.2 A flows through a conductor. Calculate how much charge passes through any cross-section of the conductor in 20 seconds. Chapter 1, Solution 4  $q = it = 3.2 \times 20 = 64 \text{ C}$  Chapter 1, Problem 5. Determine the total charge transferred over the time interval of  $0 \leq t \leq 10 \text{ s}$  when  $i(t) = t \text{ A}$ . Chapter 1, Solution 5  $q = \int_0^{10} i(t) dt = \int_0^{10} t dt = 25 \text{ C}$

2 4 0 0 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 1, Problem 6. The charge entering a certain element is shown in Fig. 1.23. Find the current at: (a)  $t = 1 \text{ ms}$  (b)  $t = 6 \text{ ms}$  (c)  $t = 10 \text{ ms}$  Figure 1.23 Chapter 1, Solution 6 (a) At  $t = 1 \text{ ms}$ ,  $i = \frac{dq}{dt} = \frac{40 \text{ C}}{1 \text{ ms}} = 40 \text{ A}$  (b) At  $t = 6 \text{ ms}$ ,  $i = \frac{dq}{dt} = \frac{-20 \text{ C}}{1 \text{ ms}} = -20 \text{ A}$  (c) At  $t = 10 \text{ ms}$ ,  $i = \frac{dq}{dt} = \frac{0 \text{ C}}{1 \text{ ms}} = 0 \text{ A}$

2 4 0 0 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 1, Problem 7. The charge flowing in a wire is plotted in Fig. 1.24. Sketch the corresponding current. Figure 1.24 Chapter 1, Solution 7  $i = \frac{dq}{dt} = -25 \text{ A}$  for  $0 < t < 1$   $i = \frac{dq}{dt} = 25 \text{ A}$  for  $1 < t < 2$   $i = \frac{dq}{dt} = -25 \text{ A}$  for  $2 < t < 3$   $i = \frac{dq}{dt} = 25 \text{ A}$  for  $3 < t < 4$

1. 6196 mA -1. 0202 mA -2. 461 mA 3 mA -2. 423 mA

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 54.

Find the mesh currents  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit in Fig. 3. 99. Figure 3. 99 Chapter 3, Solution 54 Let the mesh currents be in mA. For mesh 1,  $12 + 10 + 2i_1 - i_2 = 0$   $\Rightarrow 2i_1 - i_2 = -22$  For mesh 2,  $10 + 3i_2 - i_1 - i_3 = 0$  For mesh 3,  $12 + 2i_3 - i_2 = 0$   $\Rightarrow$  (1)  $10 = i_1 + 3i_2 - i_3$  (2)  $12 = i_2 + 2i_3$  (3) Putting (1) to (3) in matrix form leads to  $\begin{bmatrix} 2 & -1 & 0 \\ -1 & 2 & -1 \\ 0 & 1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -22 \\ 10 \\ 12 \end{bmatrix}$  Using MATLAB,  $\gg A \setminus B$   $\Rightarrow i_1 = 5.25$  mA,  $i_2 = 8.5$  mA,  $i_3 = 10.25$  mA

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 55. In the circuit of Fig. 3. 100, solve for  $i_1$ ,  $i_2$ , and  $i_3$ . Figure 3. 100 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Solution 55

10 V b  $I_2$   $i_1$   $I_2$  + c 1A 1A 4A 6?  $I_1$  d  $I_3$  2?  $i_2$  4A a  $I_2$  ?  $I_4$   $i_3$  4? +-  $I_3$   $I_4$  8V 0

It is evident that  $I_1 = 4$  A For mesh 4,  $12(I_4 - I_1) + 4(I_4 - I_3) - 8 = 0$

$6(I_2 - I_1) + 10 + 2I_3 + 4(I_3 - I_4) = 0$  or  $-3I_1 + 3I_2 + 3I_3 - 2I_4 = -5$  (1) (2) (3) (4) For the supermesh At node c,

$I_2 = I_3 + 1$  Solving (1), (2), (3), and (4) yields,  $I_1 = 4$  A,  $I_2 = 3$  A,  $I_3 = 2$  A, and  $I_4 = 4$  A At node b, At node a, At node 0,  $i_1 = I_2 - I_1 = -1$  A  $i_2 = 4 - I_4 = 0$  A  $i_3 = I_4 - I_3 = 2$  A

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 56. Determine  $v_1$  and  $v_2$  in the circuit of Fig. 3. 101.

Figure 3. 101 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without

For loop 1,  $12 = 4i_1 - 2i_2 - 2i_3$  which leads to  $6 = 2i_1 - i_2 - i_3$  For loop 2,  $0 = 6i_2 - 2i_1 - 2i_3$  which leads to  $0 = -i_1 + 3i_2 - i_3$  For loop 3,  $0 = 6i_3 - 2i_1 - 2i_2$  which leads to  $0 = -i_1 - i_2 + 3i_3$  In matrix form (1), (2), and (3) become,

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

$(1) \quad (2) \quad (3)$

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

$2i_1 - i_2 - i_3 = 6, -i_1 + 3i_2 - i_3 = 0, -i_1 - i_2 + 3i_3 = 0$ , therefore  $i_2 = i_3 = 24/8 = 3A$ ,  $i_1 = 0$

$v_1 = 2i_2 = 6$  volts,  $v = 2i_3 = 6$  volts

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 57. In the circuit in Fig. 3. 102, find the values of  $R$ ,  $V_1$ , and  $V_2$  given that  $i_o = 18 \text{ mA}$ . Figure 3. 102 Chapter 3, Solution 57 Assume  $R$  is in kilo-ohms.  $V_2 = 4k \times 18\text{mA} = 72\text{V}$ ,  $V_1 = 100 \text{ V}$ ,  $V_2 = 100 \text{ V} - 72 = 28\text{V}$  Current through  $R$  is  $i_R = i_o$ ,  $V_1 = i_R R$ ,  $100 = (18) R$ ,  $R = 100/18 = 5.56 \text{ k}\Omega$ . This leads to  $R = 84/26 = 3.23 \text{ k}\Omega$ .

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 58. Find  $i_1$ ,  $i_2$ , and  $i_3$  the circuit in Fig. 3. 103. Figure 3. 103 Chapter 3, Solution 58  $30 \angle i_2 \ 30 \angle 10 \angle 10 \angle 30 \angle i_1 + i_3 \ 20 \text{ V}$  - For loop 1,  $120 + 40i_1 - 10i_2 = 0$ , which leads to  $-12 = 4i_1 - i_2$  For loop 2,  $50i_2 - 10i_1 - 10i_3 = 0$ , which leads to  $-i_1 + 5i_2 - i_3 = 0$  For loop 3,  $-120 - 10i_2 + 40i_3 = 0$ , which leads to  $12 = -i_2 + 4i_3$  Solving (1), (2), and (3), we get,  $i_1 = -3\text{A}$ ,  $i_2 = 0$ , and  $i_3 = 3\text{A}$  (1) (2) (3) PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 59. Rework Prob. 3. 30 using mesh analysis. Chapter 3, Problem 30. Using nodal analysis, find  $v_o$  and  $i_o$  in the circuit of Fig. 3. 79. Figure 3. 79 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Solution 59  $40 \angle - \angle I_0 \ 10 \angle 20 \angle i_2 \ 120 \text{ V} + 100\text{V} + i_1 - 4v_0 + - 2I_0 \ i_2 \ i_3 \ v_0 \ 80 \angle - i_3$  For loop 1,  $-100 + 30i_1 - 20i_2 + 4v_0 = 0$ , where  $v_0 = 80i_3$  or  $5 = 1. 5i_1 - i_2 + 16i_3$  For the supermesh,  $60i_2 - 20i_1 - 120 + 80i_3 - 4v_0 = 0$ , where  $v_0 = 80i_3$  or  $6 = -i_1 + 3i_2 - 12i_3$  Also,  $2I_0 = i_3 - i_2$  and  $I_0 = i_2$ ,

hence,  $3i_2 = i_3 + 3 + 2 + 32 + \dots + 1 + 3 + 12 + \dots + 1 + 3 + 0 + \dots + i_1 + \dots + 10 + \dots + i_2$   
 $= 6 + 2 + \dots + i_3 + \dots + 0 + \dots + (1) (2) (3)$  From (1), (2), and (3),  $3 + 32 + 3$   
 $10 + 32 + 3 + 2 + 10 + \dots = 1 + 3 + 12 = 5$ ,  $2 = 1 + 6 + 12 = 28$ ,  $3 = 1 + 3 + 6 = 10$   
 $84 + 0 + 3 + 1 + 0 + 0 + 1 + 0 + 3 + 0 + 10 = i_2 = 2/5 = -28/5 = -5.6$  A  $v_0 = 8i_3 = (-84/5)80$   
 $= -1.344$  kvolts PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 60. Calculate the power dissipated in each resistor in the circuit in Fig. 3. 104. Figure 3. 104 Chapter 3, Solution 60  $0.5i_0 + 4 + 10 + V + 8 + v_1 + 1 + 10 + V + v_2 + 2 + i_0$  At node 1,  $(v_1/1) + (0.5v_1/1) = (10 - v_1)/4$ , which leads to  $v_1 = 10/7$  At node 2,  $(0.5v_1/1) + ((10 - v_2)/8) = v_2/2$  which leads to  $v_2 = 22/7$   $P_1 = (v_1)^2/1 = 2.041$  watts,  $P_2 = (v_2)^2/2 = 4.939$  watts  $P_4 = (10 - v_1)^2/4 = 18.38$  watts,  $P_8 = (10 - v_2)^2/8 = 5.88$  watts PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc.

All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 61. Calculate the current gain  $i_o/i_s$  in the circuit of Fig. 3.



105. Figure 3. 105 Chapter 3, Solution 61  $v_1$  is 20 V  $v_2$  10 V  $i_0$  +  $v_0$  - 30 V -  
+ 5 $v_0$  40 V

At node 1,  $i_s = (v_1/30) + ((v_1 - v_2)/20)$  which leads to  $60i_s = 5v_1 - 3v_2$  But  $v_2 = -5v_0$  and  $v_0 = v_1$  which leads to  $v_2 = -5v_1$  Hence,  $60i_s = 5v_1 + 15v_1 = 20v_1$  which leads to  $v_1 = 3i_s$ ,  $v_2 = -15i_s$   $i_0 = v_2/50 = -15i_s/50$  which leads to  $i_0/i_s = -15/50 = -0.3$  (1) PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 62. Find the mesh currents  $i_1$ ,  $i_2$ , and  $i_3$  in the network of Fig. 3. 106. Figure 3. 106 Chapter 3, Solution 62 4 k $\Omega$  A 8 k $\Omega$  B 2 k $\Omega$  100V + -  
 $i_1$   $i_2$   $i_3$  + - 40 V We have a supermesh. Let all R be in k $\Omega$ , i in mA, and v in volts. For the supermesh,  $-100 + 4i_1 + 8i_2 + 2i_3 + 40 = 0$  or  $30 = 2i_1 + 4i_2 + i_3$  At node A, At node B,  $i_1 + 4 = i_2$   $i_2 = 2i_1 + i_3$  (1) (2) (3) Solving (1), (2), and (3), we get  $i_1 = 2$  mA,  $i_2 = 6$  mA, and  $i_3 = 2$  mA. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc.

All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 63. Find  $v_x$ , and  $i_x$  in the circuit shown in Fig. 3. 107.

Figure 3. 107 Chapter 3, Solution 63  $10 \text{ V} + - i_1 i_2 + - 4i_x$  For the supermesh,  $-50 + 10i_1 + 5i_2 + 4i_x = 0$ , but  $i_x = i_1$ .

Hence,  $50 = 14i_1 + 5i_2$  At node A,  $i_1 + 3 + (v_x/4) = i_2$ , but  $v_x = 2(i_1 - i_2)$ , hence,  $i_1 + 2 = i_2$  Solving (1) and (2) gives  $i_1 = 2.105 \text{ A}$  and  $i_2 = 4.105 \text{ A}$   
 $v_x = 2(i_1 - i_2) = -4 \text{ volts}$  and  $i_x = i_2 - 2 = 2.105 \text{ amp}$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission.

(1) (2) Chapter 3, Problem 64. Find  $v_o$ , and  $i_o$  in the circuit of Fig. 3. 108.

Figure 3. 108 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Solution 64  $i_1 50 \text{ V} + - i_2 10 \text{ V} + - i_0 10 \text{ V} + - i_2 i_1 100\text{V} + + - 4i_0 i_3 40 \text{ V} - 0.2v_0 2\text{A} B i_1 i_3$  For mesh 2,  $20i_2 - 10i_1 + 4i_0 = 0$  (1) (2) But at node A,  $i_o = i_1 - i_2$  so that (1) becomes  $i_1 = (16/6)i_2$  For the supermesh,  $-100 + 50i_1 + 10(i_1 - i_2) - 4i_0 + 40i_3 = 0$  or At node B, But,  $50 = 28i_1 - 3i_2 + 20i_3$   
 $i_3 + 0.2v_0 = 2 + i_1$   $v_0 = 10i_2$  so that (4) becomes  $i_3 = 2 + (2/3)i_2$  (3) (4) (5)  
 Solving (1) to (5),  $i_2 = 0.11764$ ,  $v_0 = 10i_2 = 1.1764 \text{ volts}$ ,  $i_0 = i_1 - i_2 =$

(5/3)i<sub>2</sub> = 196.07 mA PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 65. Use MATLAB to solve for the mesh currents in the circuit of Fig. 3. 109.

Figure 3. 109 Chapter 3, Solution 65 For mesh 1,  $-12 + 12I_1 - 6I_2 - I_4 = 0$  or  $12 = 12I_1 - 6I_2 - I_4$

$I_4$  For mesh 2, For mesh 3, For mesh 4, For mesh 5,  $-6I_1 + 16I_2 - 8I_3 - I_4 - I_5 = 0$   $-8I_2 + 15I_3 - I_5 - 9 = 0$  or  $9 = -8I_2 + 15I_3 - I_5$   $-I_1 - I_2 + 7I_4 - 2I_5 - 6 = 0$  or  $6 = -I_1 - I_2 + 7I_4 - 2I_5$   $-I_2 - I_3 - 2I_4 + 8I_5 - 10 = 0$  or  $10 = -I_2 - I_3 - 2I_4 + 8I_5$

(2) (3) (4) (5) (1) PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission.

Casting (1) to (5) in matrix form gives  $\begin{bmatrix} 12 & -6 & 0 & -1 & 0 \\ -6 & 16 & -8 & -1 & -1 \\ 0 & -8 & 15 & 0 & -1 \\ -1 & -1 & 7 & -2 & -6 \\ 0 & -1 & -1 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 12 \\ 9 \\ 6 \\ 10 \\ 0 \end{bmatrix}$  Using MATLAB we input:  $Z = [12, -6, 0, -1, 0; -6, 16, -8, -1, -1; 0, -8, 15, 0, -1; -1, -1, 7, -2, -6; 0, -1, -1, -2, 8]$  and  $V = [12; 9; 6; 10; 0]$  This leads to  $>>$

<https://assignbuster.com/solution-of-fundamental-of-electric-circuits/>

$Z = \begin{bmatrix} 12 & -6 & 0 & -1 & 0 & -6 & 16 & -8 & -1 & -1 \\ 0 & -8 & 15 & 0 & -1 & -1 & -1 & 0 & 7 & -2 \\ 0 & -1 & -1 & -2 & 8 \end{bmatrix}$ 
 $Z = \begin{bmatrix} 12 & -6 & 0 & -1 & 0 & -6 & 16 & -8 & -1 & -1 \\ 0 & -8 & 15 & 0 & -1 & -1 & -1 & 0 & 7 & -2 \\ 0 & -1 & -1 & -2 & 8 \end{bmatrix}$ 
 $V = \begin{bmatrix} 12 \\ 0 \\ 9 \\ 6 \\ 10 \end{bmatrix}$ 
 $V = \begin{bmatrix} 12 \\ 0 \\ 9 \\ 6 \\ 10 \end{bmatrix}$ 
 $I = \text{inv}(Z) * V$ 
 $I = \begin{bmatrix} 2.1701 & 1.9912 & 1.8119 & 2.0942 & 2.2489 \end{bmatrix}$ 
 Thus,  $I = [2.17, 1.9912, 1.8119, 2.094, 2.249]$

A. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 66. Write a set of mesh equations for the circuit in Fig. 3.

110. Use MATLAB to determine the mesh currents.

Figure 3. 110 For Prob. 3. 66. Chapter 3, Solution 66

The mesh equations are obtained as follows.

Putting (1) to (5) in matrix form

4 12 ? 4? ? 0 ? ? 0 ? 6 0 ? 4 18 ? ?? 32? ? ? ? ? ZI = V Using MATLAB, >> Z =  
 [30,-4,-6,-2, 0; -4, 30, 0,-2,-6; -6, 0, 18,-4, 0; -2,-2,-4, 12,-4; 0,-6, 0,-4, 18] Z=  
 30 -4 -6 -2 0 -4 30 0 -2 -6 -6 0 18 -4 0 -2 0 -2 -6 -4 0 12 -4 -4 18 >> V = [-12,-  
 16, 30, 0,-32]' V= -12 -16 30 0 -32 ;; I = inv(Z)\*V I= -0. 2779 A -1. 0488 A 1.  
 4682 A -0. 4761 A -2. 2332 A PROPRIETARY MATERIAL. © 2007 The McGraw-  
 Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 67. Obtain the node-voltage equations for the circuit in Fig. 3. 111 by inspection. Then solve for  $V_o$ . 2A 4? 2? +  $V_o$  \_ 3  $V_o$  10 ? 5? 4A Figure 3. 111 For Prob. 3. 67. Chapter 3, Solution 67 Consider the circuit below. A  $V_1$  4?  $V_2$  2? +  $V_o$  -  $V_3$  3  $V_o$  10 ? 5? 4A 0 ? ? 0. 35 ? 0. 25 ?? 2 + 3 $V_o$  ? ?? 0. 25 0. 95 ? 0. 5?  $V = ? ? 0 ? ? ? ? ? 0 ? ? ? 0. 5 0. 5 ? 6 ? ? ? ?$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Since we actually have four unknowns and only three equations, we need a constraint equation.  $V_o = V_2 - V_3$  Substituting this back into the matrix equation, the first equation becomes,  $0. 35V_1 - 3. 25V_2 + 3V_3 = -2$  This now

results in the following matrix equation,  $3 \text{ V} = 0.35 \text{ V} + 3.25 \text{ V} + 2 \text{ V} + 0.25 \text{ V}$ .  
 $95 \text{ V} = 0.5 \text{ V} + 0 \text{ V} + 0 \text{ V} + 0 \text{ V} + 6 \text{ V} + 0.5 \text{ V} + 0.5 \text{ V} + 0 \text{ V} + 0.5 \text{ V}$ . Now we can use  
 MATLAB to solve for V.  $Y = [0.35, -3.25, 3; -0.25, 0.95, -0.5; 0, -0.5, 0.5]$   
 $Y = 0.3500 \text{ } -3.2500 \text{ } 3.0000 \text{ } -0.2500 \text{ } 0.9500 \text{ } -0.5000 \text{ } 0 \text{ } -0.5000 \text{ } 0.5000$  ;  
 $I = [-2, 0, 6]'$   $I = -2 \text{ } 0 \text{ } 6$  >>  $V = \text{inv}(Y)*I$   $V = -164.105 \text{ } -77.8947 \text{ } -65.8947$   $V_o =$   
 $V_2 - V_3 = -77.89 + 65.89 = -12 \text{ V}$ . Let us now do a quick check at node 1. -  
 $3(-12) + 0.1(-164.21) + 0.25(-164.21 + 77.89) + 2 = +36 - 16.421 - 21.$   
 $58 + 2 = -0.001$ ; answer checks! PROPRIETARY MATERIAL. © 2007 The  
 McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may  
 be displayed, reproduced or distributed in any form or by any means,  
 without the prior written permission of the publisher, or used beyond the  
 limited distribution to teachers and educators permitted by McGraw-Hill for  
 their individual course preparation.

If you are a student using this Manual, you are using it without permission.  
 Chapter 3, Problem 68. Find the voltage  $V_o$  in the circuit of Fig. 3.112.  $3 \text{ A } 10 \text{ V}$   
 $+ 4 \text{ A } 40 \text{ V} \text{ } V_o \text{ } 25 \text{ V} \text{ } 20 \text{ V} \text{ } + \text{ } 24 \text{ V}$  Figure 3.112 For Prob. 3.68. Chapter 3,  
 Solution 68 Consider the circuit below. There are two non-reference nodes.  
 $3 \text{ A } V_1 \text{ } 10 \text{ V} \text{ } + V_o \text{ } 25 \text{ V} \text{ } 4 \text{ A } 40 \text{ V} \text{ } V_o \text{ } 20 \text{ V} \text{ } + \text{ } 24 \text{ V}$  PROPRIETARY MATERIAL. ©  
 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any  
 form or by any means, without the prior written permission of the publisher,  
 or used beyond the limited distribution to teachers and educators permitted  
 by McGraw-Hill for their individual course preparation. If you are a student  
 using this Manual, you are using it without permission.  $+4+3 \text{ V} = 7 \text{ V}$   $0.$   
 $125 \text{ V} = 0.1 \text{ V} + 0.1 \text{ V} + 0.19 \text{ V}$   $V = 3 + 24 / 25 = 2.04 \text{ V}$  Using

MATLAB, we get,  $\gg Y = [0.125, -0.1; -0.1, 0.19]$   $Y = 0.1250 \ -0.1000 \ -0.1000 \ 0.1900$   $\gg I = [7, -2.04]'$   $I = 7.0000 \ -2.400$  ;  $V = \text{inv}(Y) * I$   $V = 81.8909 \ 32.3636$  Thus,  $V_o = 32.36 \text{ V}$ . We can perform a simple check at node  $V_o$ ,  $3 + 0.1(32.36 - 81.89) + 0.05(32.36) + 0.04(32.36 - 24) = 3 - 4.953 + 1.618 + 0.3344 = -0.0004$ ; answer checks! PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 69. For the circuit in Fig. 3.113, write the node voltage equations by inspection. Figure 3.113 Chapter 3, Solution 69 Assume that all conductances are in mS, all currents are in mA, and all voltages are in volts.  $G_{11} = (1/2) + (1/4) + (1/1) = 1.75$ ,  $G_{22} = (1/4) + (1/4) + (1/2) = 1$ ,  $G_{33} = (1/1) + (1/4) = 1.25$ ,  $G_{12} = -1/4 = -0.25$ ,  $G_{13} = -1/1 = -1$ ,  $G_{21} = -0.25$ ,  $G_{23} = -1/4 = -0.25$ ,  $G_{31} = -1$ ,  $G_{32} = -0.25$   $i_1 = 20$ ,  $i_2 = 5$ , and  $i_3 = 10 - 5 = 5$  The node-voltage equations are:  $1.75 v_1 - 0.25 v_2 - v_3 = 20$   $-0.25 v_1 + 1 v_2 - 0.25 v_3 = 5$   $-v_1 - 0.25 v_2 + 1.25 v_3 = 5$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 70. Write the node-voltage equations by inspection and then determine values of  $V_1$  and  $V_2$  in the circuit in Fig. 3. 114.  $V_1$  is 4A 1S 2S 4ix  $V_2$  5S 2A Figure 3. 114 For Prob. 3. 70. Chapter 3, Solution 70 ? 4I x + 4 ? ? 3 0? ? 0 5 ? V = ? ? 4 I ? 2 ? x ? ? ? ? With two equations and three unknowns, we need a constraint equation,  $I_x = 2V_1$ , thus the matrix equation becomes, ? ? 5 0? ? 4? V=? ? ? 8 5? ? ? ? ? 2? This results in  $V_1 = 4/(-5) = -0.8V$  and  $V_2 = [-8(-0.8) - 2]/5 = [6.4 - 2]/5 = 0.88V$ . PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc.

All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 71. Write the mesh-current equations for the circuit in Fig. 3. 115. Next, determine the values of  $I_1$ ,  $I_2$ , and  $I_3$ . 5?  $I_1$   $I_3$  3? 10 V + \_ 1? 2? 4?  $I_2$  + \_ 5V Figure 3. 15 For Prob. 3. 71. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Solution 71 ? 9 ? 4 ? 5? ? 10 ? ?? 4 7 ? 1? I = ?? 5? ? ? ? ? ?? 5 ? 1 9 ? ? 0 ? ? ? ? ?

We can now use MATLAB solve for our currents. ; R=[9,-4,-5;-4, 7,-1;-5,-1, 9] R= 9 -4 -5 -4 7 -1 -5 -1 9 ; V=[10,-5, 0]' V= 10 -5 0 >> I= inv(R)\*V I= 2.085



A 653. 3 mA 1. 2312 A PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 72. By inspection, write the mesh-current equations for the circuit in Fig. 3. 116. Figure 3. 116 Chapter 3, Solution 72  $R_{11} = 5 + 2 = 7$ ,  $R_{22} = 2 + 4 = 6$ ,  $R_{33} = 1 + 4 = 5$ ,  $R_{44} = 1 + 4 = 5$ ,  $R_{12} = -2$ ,  $R_{13} = 0$ ,  $R_{14} = 0$ ,  $R_{21} = -2$ ,  $R_{23} = -4$ ,  $R_{24} = 0$ ,  $R_{31} = 0$ ,  $R_{32} = -4$ ,  $R_{34} = -1$ ,  $R_{41} = 0$ ,  $R_{42} = 0$ ,  $R_{43} = -1$ , we note that  $R_{ij} = R_{ji}$  for all  $i$  not equal to  $j$ .  $v_1 = 8$ ,  $v_2 = 4$ ,  $v_3 = -10$ , and  $v_4 = -4$  Hence the mesh-current equations are:  $0 \leq i_1 \leq 8 \leq 7 \leq 2 \leq 0 \leq 2 \leq 6 \leq 4 \leq 0 \leq i \leq 4 \leq 2 \leq 2 \leq 0 \leq 4 \leq 5 \leq 1 \leq i \leq 3 \leq 10 \leq 0 \leq 1 \leq 5 \leq i \leq 4 \leq 4 \leq 0$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 73. Write the mesh-current equations for the circuit in Fig. 3. 117. Figure 3. 117 Chapter 3, Solution 73  $R_{11} = 2 + 3 + 4 = 9$ ,  $R_{22} = 3 + 5 = 8$ ,  $R_{33} = 1 + 1 + 4 = 6$ ,  $R_{44} = 1 + 1 = 2$ ,  $R_{12} = -3$ ,  $R_{13} = -4$ ,  $R_{14} = 0$ ,  $R_{23} = 0$ ,  $R_{24} = 0$ ,  $R_{34} = -1$   $v_1 = 6$ ,  $v_2 = 4$ ,  $v_3 = 2$ , and  $v_4 = -3$  Hence,  $9$

$i_1 = 6 \text{ A}$ ,  $i_2 = 4 \text{ A}$ ,  $i_3 = 2 \text{ A}$ . PROPRIETARY MATERIAL. 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 74. By inspection, obtain the mesh-current equations for the circuit in Fig. 3. 11. Figure 3. 118 Chapter 3, Solution 74

$R_{11} = R_1 + R_4 + R_6$ ,  $R_{22} = R_2 + R_4 + R_5$ ,  $R_{33} = R_6 + R_7 + R_8$ ,  $R_{44} = R_3 + R_5 + R_8$ ,  $R_{12} = -R_4$ ,  $R_{13} = -R_6$ ,  $R_{14} = 0$ ,  $R_{23} = 0$ ,  $R_{24} = -R_5$ ,  $R_{34} = -R_8$ , again, we note that  $R_{ij} = R_{ji}$  for all  $i$  not equal to  $j$ . The input voltage vector is  $\mathbf{V} = [V_1 \ 0 \ 0 \ V_4]^T$ . The input voltage vector is  $\mathbf{V} = [V_1 \ 0 \ 0 \ V_4]^T$ . PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Problem 75. Use PSpice to solve Prob. 3. 58. Chapter 3, Problem 58 Find  $i_1$ ,  $i_2$ , and  $i_3$

the circuit in Fig. 3. 103. Figure 3. 103 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 3, Solution 75 \* Schematics Netlist \* R\_R4 R\_R2 R\_R1 R\_R3 R\_R5 V\_V4 v\_V3 v\_V2 v\_V1 \$N\_0002 \$N\_0001 30 \$N\_0001 \$N\_0003 10 \$N\_0005 \$N\_0004 30 \$N\_0003 \$N\_0004 10 \$N\_0006 \$N\_0004 30 \$N\_0003 0 120V \$N\_0005 \$N\_0001 0 0 \$N\_0006 0 0 \$N\_0002 0 3 i1 i2 Clearly,  $i_1 = -3$  amps,  $i_2 = 0$  amps, and  $i_3 = 3$  amps, which agrees with the answers in Problem 3. 44. Chapter 3, Problem 76. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Use PSpice to solve Prob. 3. 27. Chapter 3, Problem 27 Use nodal analysis to determine voltages  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit in Fig. 3. 76. Figure 3. 76 Chapter 3, Solution 76 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution

to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. \*

Schematics Netlist \* I\_I2 R\_R1 R\_R3 R\_R2 F\_F1 VF\_F1 R\_R4 R\_R6 I\_I1 R\_R5 0  
 \$N\_0001 DC 4A \$N\_0002 \$N\_0001 0. 25 \$N\_0003 \$N\_0001 1 \$N\_0002  
 \$N\_0003 1 \$N\_0002 \$N\_0001 VF\_F1 3 \$N\_0003 \$N\_0004 0V 0 \$N\_0002 0. 5  
 0 \$N\_0001 0. 5 0 \$N\_0002 DC 2A 0 \$N\_0004 0. 25 Clearly,  $v_1 = 625$  mVolts,  
 $v_2 = 375$  mVolts, and  $v_3 = 1.625$  volts, which agrees with the solution  
 obtained in Problem 3. 27. Chapter 3, Problem 77. Solve for  $V_1$  and  $V_2$  in the  
 circuit of Fig. 3. 119 using PSpice. PROPRIETARY MATERIAL. 2007 The  
 McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may  
 be displayed, reproduced or distributed in any form or by any means,  
 without the prior written permission of the publisher, or used beyond the  
 limited distribution to teachers and educators permitted by McGraw-Hill for  
 their individual course preparation. If you are a student using this Manual,  
 you are using it without permission. 2 ix  $V_1$  5?  $V_2$  5A 2? ix 1? 2A Figure 3.  
 119 For Prob. 3. 77. Chapter 3, Solution 77 PROPRIETARY MATERIAL. © 2007  
 The McGraw-Hill Companies, Inc.

All rights reserved. No part of this Manual may be displayed, reproduced or  
 distributed in any form or by any means, without the prior written permission  
 of the publisher, or used beyond the limited distribution to teachers and  
 educators permitted by McGraw-Hill for their individual course preparation. If  
 you are a student using this Manual, you are using it without permission. As  
 a check we can write the nodal equations,  $? 1. 7 ? 0. 2 ? ? 5 ? V = ? ? ? ? 1. 2 1.$

2 ? ? ? ? ? 2? Solving this leads to  $V_1 = 3.111 \text{ V}$  and  $V_2 = 1.4444 \text{ V}$ . The answer checks!

Chapter 3, Problem 78. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Solve Prob. 3. 20 using PSpice. Chapter 3, Problem 20 For the circuit in Fig. 3. 9, find  $V_1$ ,  $V_2$ , and  $V_3$  using nodal analysis. Figure 3. 69 Chapter 3, Solution 78 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. The schematic is shown below.

When the circuit is saved and simulated the node voltages are displaced on the pseudocomponents as shown. Thus,  $V_1 = 3 \text{ V}$ ,  $V_2 = 4.5 \text{ V}$ ,  $V_3 = 15 \text{ V}$ , . Chapter 3, Problem 79. Rework Prob. 3. 28 using PSpice. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission.

Chapter 3, Problem 28 Use MATLAB to find the voltages at nodes a, b, c, and d in the circuit of Fig. 3. 77. Figure 3. 77 Chapter 3, Solution 79 The schematic is shown below. When the circuit is saved and simulated, we obtain the node voltages as displayed. Thus,  $V_a = 5.278\text{ V}$ ,  $V_b = 10.28\text{ V}$ ,  $V_c = 0.6944\text{ V}$ ,  $V_d = 26.88\text{ V}$  Chapter 3, Problem 80. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Find the nodal voltage  $v_1$  through  $v_4$  in the circuit in Fig. 3. 120 using PSpice. Figure 3. 120 Chapter 3, Solution 80 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. \* Schematics Netlist \*

```
H_H1 VH_H1 I_I1 V_V1 R_R4 R_R1 R_R2 R_R5 R_R3 $N_0002 $N_0003 VH_H1
6 0 $N_0001 0V $N_0004 $N_0005 DC 8A $N_0002 0 20V 0 $N_0003 4
$N_0005 $N_0003 10 $N_0003 $N_0002 12 0 $N_0004 1 $N_0004 $N_0001 2
```

Clearly,  $v_1 = 84\text{ volts}$ ,  $v_2 = 4\text{ volts}$ ,  $v_3 = 20\text{ volts}$ , and  $v_4 = -5.333\text{ volts}$  Chapter 3, Problem 81. Use PSpice to solve the problem in Example 3. 4

<https://assignbuster.com/solution-of-fundamental-of-electric-circuits/>

PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Example 3. 4 Find the node voltages in the circuit of Fig. 3. 12. Figure 3. 12 Chapter 3, Solution 81 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Clearly,  $v_1 = 26.67$  volts,  $v_2 = 6.667$  volts,  $v_3 = 173.33$  volts, and  $v_4 = -46.67$  volts which agrees with the results of Example 3. 4. This is the netlist for this circuit. \* Schematics Netlist \* R\_R1 R\_R2 R\_R3 R\_R4 R\_R5 I\_I1 V\_V1 E\_E1 0 \$N\_0001 2 \$N\_0003 \$N\_0002 6 0 \$N\_0002 4 0 \$N\_0004 1 \$N\_0001 \$N\_0004 3 0 \$N\_0003 DC 10A \$N\_0001 \$N\_0003 20V \$N\_0002 \$N\_0004 \$N\_0001 \$N\_0004 3 Chapter 3, Problem 82. If the Schematics Netlist for a network is as follows, draw the network. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted

by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

R\_R1 R\_R2 R\_R3 R\_R4  
R\_R5 V\_VS I\_IS F\_F1 VF\_F1 E\_E1 1 2 2 3 1 4 0 1 5 3 2 0 0 4 3 0 1 3 0 2 2K 4K  
8K 6K 3K DC DC VF\_F1 0V 1 100 4 2 3 3 Chapter 3, Solution 82  $2i_0 + v_0 - 3$   
 $k? 1 4A 2 k? 2 + 3v_0 3 6 k? 4 4 k? 8 k? 100V + - 0$

This network corresponds to the Netlist. Chapter 3, Problem 83. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. The following program is the Schematics Netlist of a particular circuit.

Draw the circuit and determine the voltage at node 2. R\_R1 R\_R2 R\_R3 R\_R4  
V\_VS I\_IS 1 2 2 3 1 2 2 0 3 0 0 0 20 50 70 30 20V DC 2A Chapter 3, Solution  
83 The circuit is shown below.  $1 20 ? 2 70 ? 3 20 V + - 50 ? 2A 30 ? 0$  When  
the circuit is saved and simulated, we obtain  $v_2 = -12.5$  volts Chapter 3,  
Problem 84. Calculate  $v_o$  and  $i_o$  in the circuit of Fig. 3. 121. Figure 3. 121  
Chapter 3, Solution 84 From the output loop,  $v_0 = 50i_0 \times 20 \times 10^3 = 106i_0$  (1)  
From the input loop,  $3 \times 10^{-3} + 4000i_0 - v_0/100 = 0$  (2) From (1) and (2) we  
get,  $i_0 = 0.5?$

A and  $v_0 = 0.5$  volt. Chapter 3, Problem 85. PROPRIETARY MATERIAL. ©  
2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this  
Manual may be displayed, reproduced or distributed in any form or by any  
means, without the prior written permission of the publisher, or used beyond  
<https://assignbuster.com/solution-of-fundamental-of-electric-circuits/>



the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. An audio amplifier with resistance  $9\Omega$  supplies power to a speaker.

In order that maximum power is delivered, what should be the resistance of the speaker? Chapter 3, Solution 85 The amplifier acts as a source.  $R_s = 9\Omega$  For maximum power transfer,  $R_L = R_s = 9\Omega$  Chapter 3, Problem 86. For the simplified transistor circuit of Fig. 3. 122, calculate the voltage  $v_o$ . Figure 3. 122 Chapter 3, Solution 86 Let  $v_1$  be the potential across the  $2\text{ k}\Omega$  resistor with plus being on top. Then,  $[(0.03 - v_1)/1\text{ k}] + 400i = v_1/2\text{ k}$  (1) Assume that  $i$  is in mA. But,  $i = (0.03 - v_1)/1$  Combining (1) and (2) yields,  $v_1 = 29.963\text{ mVolts}$  and  $i = 37.4\text{ nA}$ , therefore,  $v_o = -5000 \times 400 \times 37.4 \times 10^{-9} = -74.8\text{ mvolts}$  (2) Chapter 3, Problem 87. For the circuit in Fig. 3. 123, find the gain  $v_o/v_s$ . PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

Figure 3. 123 Chapter 3, Solution 87  $v_1 = 500(v_s)/(500 + 2000) = v_s/5$   $v_o = -400(60v_1)/(400 + 2000) = -40v_1 = -40(v_s/5) = -8v_s$ , Therefore,  $v_o/v_s = -8$  Chapter 3, Problem 88. Determine the gain  $v_o/v_s$  of the transistor amplifier circuit in Fig. 3. 124. Figure 3. 124 Chapter 3, Solution 88 Let  $v_1$  be the potential at the top end of the  $100\text{-}\Omega$  resistor.  $(v_s - v_1)/200 = v_1/100 +$

$(v_1 - 10^{-3}v_0)/2000$  For the right loop,  $v_0 = -40i_0(10,000) = -40(v_1 - 10^{-3})10,000/2000$ , or,  $v_0 = -200v_1 + 0.2v_0 = -4 \times 10^{-3}v_0$  (2) (1) Substituting (2) into (1) gives,  $(v_s + 0.004v_1)/2 = -0.004v_0 + (-0.04v_1 - 0.001v_0)/20$  This leads to  $0.125v_0 = 10v_s$  or  $(v_0/v_s) = 10/0.125 = -80$  Chapter 3, Problem 89. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. For the transistor circuit shown in Fig. 3.125, find  $I_B$  and  $V_{CE}$ . Let  $\beta = 100$  and  $V_{BE} = 0.7\text{V}$ .  $-3\text{V} + -1\text{k}\Omega \cdot 0.7\text{V} + 100\text{k}\Omega \parallel 15\text{V}$  Figure 3.125 For Prob. 3.89. Chapter 3, Solution 89 Consider the circuit below.  $-0.7\text{V}$   $C + 100\text{k}\Omega + I_C$   $V_{CE}$   $-3\text{V} + -E$  For the left loop, applying KVL gives  $V_{BE} = 0.7\text{V} + 3\text{V} + 0.7\text{V} + 100 \times 10^3 I_B + V_{BE} = 0$   $IB = 30\text{ }\mu\text{A}$  > For the right loop,  $\beta V_{CE} + 15\text{V} - I_C(1 \times 10^3) = 0$  But  $I_C = \beta I_B = 100 \times 30\text{ }\mu\text{A} = 3\text{mA}$   $15\text{V} - 1\text{k}\Omega V_{CE} = 3 \times 10^{-3} \times 10^3 = 12\text{V}$  Chapter 3, Problem 90. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Calculate  $v_s$  for the transistor in Fig. 3.126, given that  $v_o = 4\text{V}$ ,  $\beta = 150$ ,  $V_{BE} = 0.7\text{V}$ . Figure 3.126 Chapter 3, Solution 90  $1\text{k}\Omega$   $10\text{k}\Omega$   $I_B + V_{BE} + V_{CE} - i_2 + v_s + - - i_1$   $18\text{V}$

$500 \text{ V} + V_0 - I_E$  - For loop 1,  $-v_s + 10k(I_B) + V_{BE} + I_E(500) = 0 = -v_s + 0. + 10,000I_B + 500(1 + \beta)I_B$  which leads to  $v_s + 0.7 = 10,000I_B + 500(151)I_B = 85,500I_B$  But,  $v_0 = 500I_E = 500 \times 151I_B = 4$  which leads to  $I_B = 5.298 \times 10^{-5}$  Therefore,  $v_s = 0.7 + 85,500I_B = 5.23 \text{ volts}$  Chapter 3, Problem 91. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. For the transistor circuit of Fig. 3. 127, find  $I_B$ ,  $V_{CE}$ , and  $v_o$ . Take  $\beta = 200$ ,  $V_{BE} = 0.7\text{V}$ . Figure 3. 127 Chapter 3, Solution 91 We first determine the Thevenin equivalent for the input circuit.  $R_{Th} = 6k \parallel 2k = 6 \times 2 / 8 = 1.5k\Omega$  and  $V_{Th} = 2(3)/(2+6) = 0.75 \text{ volts}$   $5k \parallel 1.5k \parallel I_B + V_{BE} + V_{CE} - i_2 + + 0.75 \text{ V} - - i_1 9\text{V}$   $400 \text{ V} - I_E$  B - For loop 1,  $-0.75 + 1.5kI_B + V_{BE} + 400I_E = 0 = -0.75 + 0.7 + 1500I_B + 400(1 + \beta)I_B$   $I_B = 0.05/81,900 = 0.61 \mu\text{A}$   $v_0 = 400I_E = 400(1 + \beta)I_B = 49 \text{ mV}$  B For loop 2,  $-400I_E - V_{CE} - 5kI_C + 9 = 0$ , but,  $I_C = \beta I_B$  and  $I_E = (1 + \beta)I_B$   $V_{CE} = 9 - 5k\beta I_B - 400(1 + \beta)I_B = 9 - 0.659 = 8.641 \text{ volts}$  B B Chapter 3, Problem 92. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission.

Find  $I_B$  and  $V_C$  for the circuit in Fig. 3. 128. Let  $\beta = 100$ ,  $V_{BE} = 0.7\text{V}$ . Figure 3. 128 Chapter 3, Solution 92

$10\text{ k}\Omega$   $I_1$   $5\text{ k}\Omega$   $V_C$   $I_C$   $I_B$   $V_{BE}$   $4\text{ k}\Omega$   $V_{CE}$   $-12\text{V}$

$V_0 - I_E - I_1 = I_B + I_C = (1 + \beta)I_B$  and  $I_E = I_B + I_C = I_1$  Applying KVL around the outer loop,

$$4\text{ k}\Omega I_E + V_{BE} + 10\text{ k}\Omega I_B + 5\text{ k}\Omega I_1 = 12$$

$$12 - 0.7 = 5\text{ k}\Omega(1 + \beta)I_B + 10\text{ k}\Omega I_B + 4\text{ k}\Omega(1 + \beta)I_B = 919\text{ k}\Omega I_B$$

$$I_B = 11.3/919\text{ k} = 12.296\text{ }\mu\text{A}$$

Also,

$$12 = 5\text{ k}\Omega I_1 + V_C$$

which leads to  $V_C = 12 - 5\text{ k}\Omega(101)I_B = 5.791\text{ volts}$

Chapter 3, Problem 93 Rework Example 3. 1 with hand calculation. PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission.

In the circuit in Fig. 3. 34, determine the currents  $i_1$ ,  $i_2$ , and  $i_3$ . Figure 3. 34 Chapter 3, Solution 93

$v_1$   $i_1$   $2\text{ }\Omega$   $i_2$   $3\text{V}$   $v_0$   $v_2$   $i_3$   $+8\text{ }\Omega$   $2\text{ }\Omega$   $3\text{V}$   $v_0$   $i_2$   $4\text{ }\Omega$   $i$   $v_0$   $+v_2$   $24\text{V}$   $+v_1$   $-$   $-$   $-$  (a)

(b) From (b),  $-v_1 + 2i - 3v_0 + v_2 = 0$  which leads to  $i = (v_1 + 3v_0 - v_2)/2$

At node 1 in (a),  $((24 - v_1)/4) = (v_1/2) + ((v_1 + 3v_0 - v_2)/2) + ((v_1 - v_2)/1)$ , where  $v_0 = v_2$  or  $24 = 9v_1$  which leads to  $v_1 = 2.667\text{ volts}$

At node 2,  $((v_1 - v_2)/1) + ((v_1 + 3v_0 - v_2)/2) = (v_2/8) + v_2/4$ ,  $v_0 = v_2$   $v_2 = 4v_1 = 10.66\text{ volts}$

Now we can solve for the currents,  $i_1 = v_1/2 = 1.333\text{ A}$ ,  $i_2 = 1.333\text{ A}$ , and  $i_3 = 2.6667\text{ A}$ . PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher,

or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 1. Calculate the current  $i_o$  in the circuit of Fig. 4. 69. What does this current become when the input voltage is raised to 10 V? Figure 4. 69 Chapter 4, Solution 1.  $+ ? 8 (5 + 3) = 4? , i = i_o = 1 \text{ A} = 1 + 4 \text{ A} = 5 \text{ A} \Rightarrow i_o = 0.1 \text{ A}$  Since the resistance remains the same we get  $i = 10/5 = 2 \text{ A}$  which leads to  $i_o = (1/2)i = (1/2)2 = 1 \text{ A}$ . PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 2.

Find  $v_o$  in the circuit of Fig. 4. 70. If the source current is reduced to  $1 \text{ A}$ , what is  $v_o$ ? Figure 4. 70 Chapter 4, Solution 2.  $6 (4 + 2) = 3? , i_1 = i_2 = i_o = 1 \text{ A} \Rightarrow v_o = 2i_o = 0.5 \text{ V}$  If  $i_s = 1 \text{ A}$ , then  $v_o = 0.5 \text{ V}$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 3. (a) In the circuit in Fig. 4. 71, calculate  $v_o$  and  $i_o$  when  $v_s = 1 \text{ V}$ . (b) Find  $v_o$  and  $i_o$  when  $v_s = 10 \text{ V}$ . (c) What are  $v_o$  and  $i_o$  when

each of the  $1\text{-}\Omega$  resistors is replaced by a  $10\text{-}\Omega$  resistor and  $v_s = 10\text{ V}$ ? Figure 4. 71 Chapter 4, Solution 3. + ? +  $v_o$  + ? (a) We transform the Y sub-circuit to the equivalent ? .  $3R \parallel 3R \parallel 3R = R$ ,  $R + R = 2R$ ,  $2R \parallel 3R = \frac{6R}{5}$ ,  $\frac{6R}{5} \parallel 4R = \frac{12R}{11}$  vs  $v_o =$  independent of R  $i_o = v_o/(R)$  When  $v_s = 1\text{V}$ ,  $v_o = 0.5\text{V}$ ,  $i_o = 0.5\text{A}$  (b) When  $v_s = 10\text{V}$ ,  $v_o = 5\text{V}$ ,  $i_o = 5\text{A}$  (c) When  $v_s = 10\text{V}$  and  $R = 10\Omega$   $v_o = 5\text{V}$ ,  $i_o = 10/(10) = 1\text{A}$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 4. Use linearity to determine  $i_o$  in the circuit in Fig. 4. 72. Figure 4. 72 Chapter 4, Solution 4.

If  $i_o = 1$ , the voltage across the  $6\Omega$  resistor is  $6\text{V}$  so that the current through the  $3\Omega$  resistor is  $2\text{A}$ . +  $v_1$   $3 \parallel 6 = 2\Omega$ ,  $v_o = 3(4) = 12\text{V}$ ,  $i_1 =$  Hence  $I_s = 3 + 3 = 6\text{A}$  If  $I_s = 6\text{A}$   $I_s = 9\text{A}$   $i_o = 1$   $i_o = 9/6 = 1.5\text{A}$   $v_o = 3\text{A}$ . 4 PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 5. For the circuit in Fig. 4. 73, assume  $v_o = 1\text{ V}$ , and use linearity to find the actual value of  $v_o$ . Figure 4. 73 Chapter 4, Solution 5. + ? If  $v_o = 1\text{V}$ , ?  $1\Omega \parallel V_1 = ? \parallel 1 = 2\text{V}$  ?  $3\Omega \parallel 10\Omega \parallel 2\Omega$   $V_s = 2\text{V}$  ? +  $v_1 = 3\text{V}$  ? If  $v_s =$

10 3  $v_o = 1$   $v_o = 3 \times 15 = 4.5$  V 10 Then  $v_s = 15$  PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved.

No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation. If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 6.

For the linear circuit shown in Fig. 4. 74, use linearity to complete the following table. Experiment 1 2 3 4  $V_s$  12 V -1V - $V_o$  4V 16 V --2V +  $V_s$  + \_ Linear Circuit  $V_o$  - Figure 4. 74

For Prob. 4. 6. Chapter 4, Solution 6. Due to linearity, from the first experiment, 1  $V_o = V_s$  3 Applying this to other experiments, we obtain:  
Experiment 2 3 4  $V_s$  48 1V -6 V  $V_o$  16 V 0. 333 V -2V PROPRIETARY MATERIAL. © 2007 The McGraw-Hill Companies, Inc. All rights reserved. No part of this Manual may be displayed, reproduced or distributed in any form or by any means, without the prior written permission of the publisher, or used beyond the limited distribution to teachers and educators permitted by McGraw-Hill for their individual course preparation.

If you are a student using this Manual, you are using it without permission. Chapter 4, Problem 7. Use linearity and the assumption that  $V_o = 1$  V to find the actual value of  $V_o$  in Fig. 4. 75. . 1? 4? + 4V + \_ 3? 2?  $V_o$  \_ Figure 4. 75

For Prob. 4. 7. Chapter 4, Solution 7. If  $V_o = 1$  V, then the current through the 2-? and 4-? resistors is  $? = 0.5$ . The voltage across the 3-? resistor is  $? (4 + 2) = 3$  V. The total current through the 1-? resistor is  $0.5 + 3/3 = 1.5$  A. Hence the