

The three phase pwm inverter engineering essay

[Engineering](#)



**ASSIGN
BUSTER**

London South Bank University

Department of Engineering and Design,

BEng (Hons) Electrical/Electronic Engineering

Power Systems, Energy converters & Drives Report

Author: Maharishan Saravanapavananthan ID: 3012401 Academic Session:

4th year BEng(Hons) Supervisor: Dr M Shirkoohi Course Title:

Electrical/Electronic Engineering (SES) Mode of Study: Full Time

Contents Page:

Aims/Objectives: Page 2 Introduction: Page 2 Experimental Process: Page

3 Inverter supply: Page 3 Inverter output: Page 5 Conclusion: Page 9 Reference:

Page 9

Aims:

To investigate the operation of the three phase pulse width modulated inverter
To understand the fundamental process of the power conversion in inverter circuit
To identify some possible problems encountered when using this type of inverter

Objectives:

To observe the supply current and voltage waveforms, determine the power factor and investigate the harmonic content of the supply current
To measure the crest factor and determine the peak current
To determine if the harmonic current affects the supply voltage
To observe the inverter output current and voltage
To investigate the change in output voltage and current with frequency
To determine the frequency of the inverter

<https://assignbuster.com/the-three-phase-pwm-inverter-engineering-essay/>

Introduction:

These days most of the inverters available in the market utilises the Pulse Width Modulation technology. The inverters based on PWM are superior in many factors compared to the other existing inverters designed using conventional technologies. The PWM inverters use Mosfets in the output switching stage. Power inverters are a circuit that is used to convert Direct current to Alternating Current. The inverter can use a DC source or a rectified AC source as it's input, there are two main types for switch mode voltage source inverters such as square wave and pulse width modulation. Square wave inverters are simple to implement although the harmonics are close to the fundamental frequency. The PWM inverters function by comparing a sinusoidal control signal at a desired frequency output with a triangle carrier signal at switching the frequency. The harmonic of the PWM inverters are located at the multiples of the carrier signal frequency which will be in the KHz range. [1]The inverter used in this exercise is a three phase pulse width modulation type with a variable output frequency, the load connected is a squirrel cage induction motor. The function of the PWM inverter is to shape and control the output voltage in magnitude and frequency in order to minimise harmonic current in the load. Although the output voltage waveform is chopping the resulting current waveform when the load is inductive, in this case for the motor, resulting sine wave is fairly good with some higher frequency ripple. Unless the inverter is powered by a battery or a DC source, the supply to the inverter is either a single or three phase AC, in this exercise single phase is used which is then rectified and smoothed, the initial conversion from AC to DC has its own problems.

Experimental Process:

The inverter is powered from a single phase AC supply which is then rectified by using a bridge rectifier, and the resulting DC is smoothed by two electrolytic capacitors. The DC is then converted to three phase AC with the frequency which can be varied. In this particular inverter the switching pulses required to produce a three phase pulse width modulated output waveform, are generated on a circuit board that plugs into the main power board. The switching pulses are fed to the drive circuit of the six Gate-turn-off Thyristors. The main transformer has been removed from the board and the low voltage power required to operate is obtained from the boxed transformer giving an output of 15-0-15 volts. The main power to drive the motor is supplied via an isolating step down transformer and an auto transformer which varies the supply voltage. The transformer isolated the circuit from the supply so that the circuit is floating with respect to ground. A current clamp is used to observe the supply and load currents and it also provides isolation between the oscilloscope and the circuit.

Inverter supply side:

The first step of this experiment is to look at the supply input to the inverter, the circuit is connected up as shown in fig 1 below. Fig 1 . Connection of supply terminal [2]The auto transformer is set to zero output voltage and switched on, meanwhile the supply voltage is increased to 41 volts. The speed of the motor can be varied by turning the potentiometer knob. The motor speed is set to maximum, fig 2 below shows the supply voltage and current waveform. voltagecurrentFig 2 supply voltage and current waveformsThe following table shows the measurements is taken from the

Voltech power analyser. Input voltage 40.47 Volts Current 0.44 Amps Power 10.21 Watts VA 17.36 Power factor 0.59 The table below is the harmonic measurements of the supply current. Fundamental 0.256 2nd harmonic 8.31% 0.021 3rd harmonic 91% 0.233 5th harmonic 73.94% 0.189 7th harmonic 50% 0.128 At maximum speed the 3rd harmonic of the supply voltage is measured which gives 0.84% of 40.47 V this equals to 0.339. The speed is then reduced to zero and measured the same harmonic again this time it shows 0.67% of 40.47 V which equals to 0.271. The crest factor of the current waveform measured using the analyser give 3.070, this is confirmed by using the crest factor ratio I_{peak}/I_{rms} formula, the I_{peak} is 1.35A and the I_{rms} is 0.44A therefore the crest factor equals $1.35/0.44 = 3.068$.

Inverter output side:

Fig 3 Load side connection [2] The auto transformer is set to zero output voltage and switched back on, the supply voltage is increased to 41 volts and the motor speed is at its maximum output voltage therefore there is a maximum frequency. Fig 4 shows the output voltage and current waveforms. F: powerpower pwmTEK0001. BMP Fig 4 Output voltage and current waveforms The output voltage is pulse width modulated however due to the time base setting of the oscilloscope not all of the pulses are viable, so in order to see the pulses the output frequency is reduced to approximately 25Hz and the time base is also reduced. Fig 5 and fig 6 below show the voltage and current waveforms at a time base of 2.5ms and 1ms. F: powerpower pwmTEK0002. BMP Fig 5 voltage and current waveforms at 2.5ms time base F: powerpower pwmTEK0003. BMP Fig 6 voltage and current

waveforms at 1ms time base The inverter is set to maximum speed and connected to the star point in order to observe the red phase voltage, fig 7 shows the voltage and current waveform of the red phase, F: powerpower pwmTEK0004. BMP Fig 7 phase voltage and current waveforms Same as before not all of the pulses are visible therefore the time base is reduced to 2. 5ms and 1ms, fig 8 and 9 shows the waveform pulses at time base of 2. 5ms and 1ms. F: powerpower pwmTEK0006. BMP Fig 8 phase voltage and current waveforms at 2. 5ms time base F: powerpower pwmTEK0007. BMP Fig 9 phase voltage and current waveform at 1ms time base A basic three-phase inverter consists of three single-phase inverter switches each connected to one of the three load terminals. The operation of the three switches is coordinated so that one switch operates at each 60 degree point of the fundamental output waveform. This creates a line-to-line output waveform that has six steps. The six-step waveform has a zero-voltage step between the positive and negative sections of the square-wave such that the harmonics that are multiples of three are eliminated as described above. When carrier-based PWM techniques are applied to six-step waveforms, the basic overall shape of the waveform is retained so that the 3rd harmonic and its multiples are cancelled.

The Inverter Efficiency:

The efficiency of the inverter output is $2.8 \times 3 = 8.4$, the input is 10watts. There are a few main power losses in the inverter which is due to the losses through the diode and the switching components.

The relationship between the inverter output voltage, current and frequency.

The output voltage, current and frequency values are measured from 10Hz to 50Hz in increments of 5Hz. The table and fig 10 and 11 below shows the inverter output voltage and current plotted against the frequency.

Frequency (Hz)	Output Voltage (volts)	Output Current (amps)
10	970	34
15	630	42
20	420	63
25	315	84
30	210	105
35	158	126
40	105	147
45	74	168
50	53	189

Conclusion:

In this experiment I have learnt that a pulse width modulation is a process of modifying the width of the pulses in a pulse train directly proportional to a small control signal, the resulting pulses will be wider if the control voltage is greater. By using sinusoid of the desired frequency as the control voltage for the PWM circuit to produce a high power waveform which an average waveform varies in a sinusoidal manner which is suitable for driving an ac squirrel cage induction motors.